



Computer Organization and Architecture **Flip flops**

ABOUT ME : MURALIKRISHNA BUKKASAMUDRAM

- M.Tech with 20 years of Experience in Teaching GATE and Engineering colleges
- IIT NPTEL Course topper in Theory of computation with 96 %
- IGIP Certified (Certification on International Engineering educator)
- GATE Qualified
- Trained more than 50 Thousand students across the country
- Area of Expertise : TOC,OS,COA,CN,DLD



Flip flops

Flip Flop



- 0 - Low (0 Volts)
- 1 - High (5 Volts)

Flip Flop is a binary storage cell.



$Q(t)$

Before Applying
inputs

$Q(t+1)$

After applying
inputs

Capable of storing 1-bits of info.

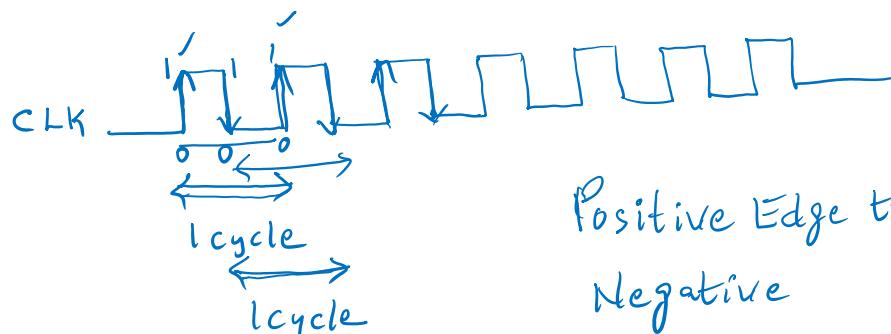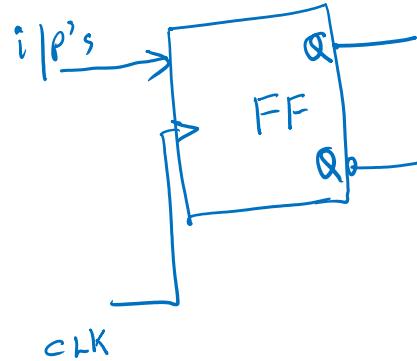


Positive Edge triggered
Negative "

Flip flops

Types of flip flops

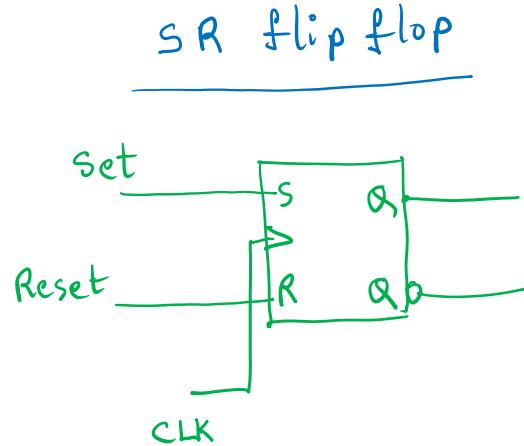- (1) SR flip flop
 - (2) D - flip flop
 - (3) T - flip flop
 - (4) JK - flip flop.
- $0 \rightarrow 0$



Characteristic Table

| clk | S | R | $Q(t+1)$ |
|-----|---|---|------------------|
| 0 | X | X | — |
| ↑ | 0 | 0 | $Q(t)$ No change |
| ↑ | 0 | 1 | 0 clear to zero |
| ↑ | 1 | 0 | 1 set to 1 |
| ↑ | 1 | 1 | Indetermination |


Excitation Table

| $Q(t)$ | $Q(t+1)$ | S | R |
|--------|----------|---|---|
| 0 | 0 | X | ✓ |
| 0 | 1 | 0 | ✓ |
| 1 | 0 | 1 | ✓ |
| 1 | 1 | X | 0 |

| S | R |
|---|---|
| 0 | 0 |
| 0 | 1 |
| 1 | 0 |
| X | 0 |

Flip flops


D - Flip Flop

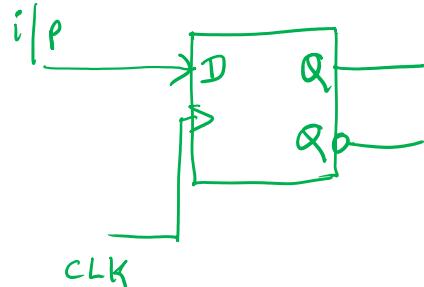

Characteristic Table

| CLK | D | $Q(t+1)$ |
|-----|---|----------|
| 0 | X | - |
| ↑ | 0 | 0 |
| ↑ | 1 | 1 |


Sequential Circuit

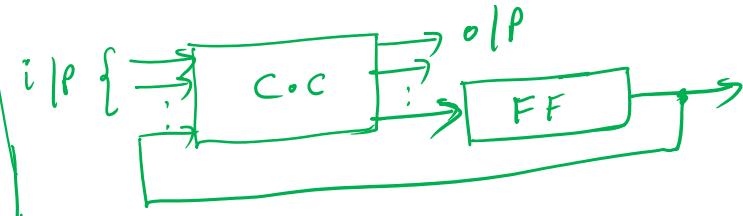

$$Q(t+1) = D$$


Excitation Table

| $Q(t)$ | $Q(t+1)$ | D |
|--------|----------|---|
| 0 → 0 | 0 | 0 |
| 0 → 1 | 1 | 1 |
| 1 → 0 | 0 | 0 |
| 1 → 1 | 1 | 1 |

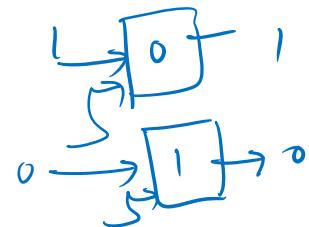

Flip flops

T-Flip Flop

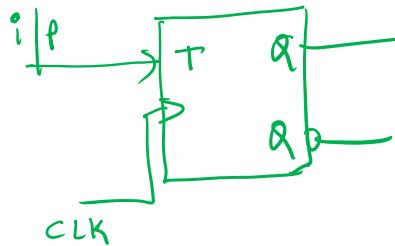

characteristic Table

| CLK | T | $Q(t+1)$ |
|-----|---|----------|
| 0 | X | - |
| ↑ | 0 | $Q(t)$ |
| ↑ | 1 | $Q'(t)$ |

Toggle

No change
complement

| T | $Q(t)$ | $Q(t+1)$ |
|---|--------|----------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 0 |

Excitation Table

| $Q(t)$ | $Q(t+1)$ | T |
|--------|----------|---|
| 0 → 0 | 0 | 0 |
| 0 → 1 | 1 | 1 |
| 1 → 0 | 0 | 1 |
| 1 → 1 | 1 | 0 |

$$Q(t+1) = Q(t) \oplus T$$

$$0 \oplus 0 = 0$$


$$1 \oplus 0 = 1$$

$$1 \oplus 1 = 0$$

$$0 \oplus 1 = 1$$

Flip flops

J K - flip flop.

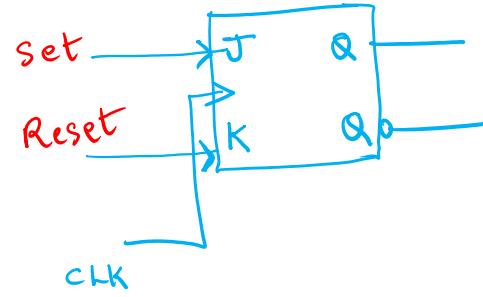

Characteristic Table

| CLK | J | K | $Q(t+1)$ |
|-----|---|---|-----------|
| 0 | X | X | — |
| ↑ | 0 | 0 | $Q(t)$ ✓ |
| ↑ | 0 | 1 | 0 ✓ |
| ↑ | 1 | 0 | 1 ✓ |
| ↑ | 1 | 1 | $Q'(t)$ ✓ |

No change
clear to 0.
set to 1
complement

| J | K |
|---|---|
| 0 | 0 |
| 1 | 0 |
| X | 0 |

| J | K |
|----|----|
| {0 | {0 |
| {1 | {1 |
| 0 | X |

Excitation Table

| $Q(t)$ | $Q(t+1)$ | J K |
|---------|----------|-----|
| 0 → 0 | 0 | 0 X |
| 0 → 1 ✓ | 1 | 1 X |
| 1 → 0 | 0 | X 1 |
| 1 → 1 ✓ | 1 | X 0 |


| $Q(t)$ | $Q(t+1)$ | J K |
|--------|----------|-----|
| 0 → 0 | 0 | 0 X |
| 0 → 1 | 1 | 1 X |
| 1 → 0 | 0 | X 1 |
| 1 → 1 | 1 | X 0 |

| J | K |
|---|---|
| 1 | 1 |
| 1 | 0 |

| J | K |
|---|---|
| 1 | 1 |
| 0 | 1 |

Flip flops

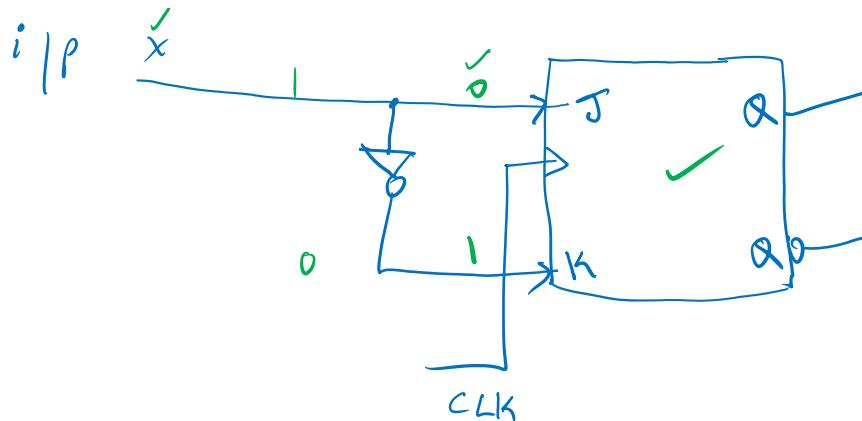
→ Consider the following JK- flip flop with an Inverter between J and K inputs.



→ Now the Circuit will function like which flip flop?

Sol :-


It is Working Like
D- flip flop.

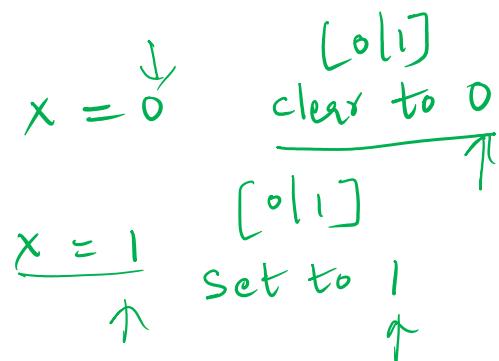

Flip flops

| $Q(t)$ | T | $Q(t+1)$ | D |
|--------|---|----------|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |

1.

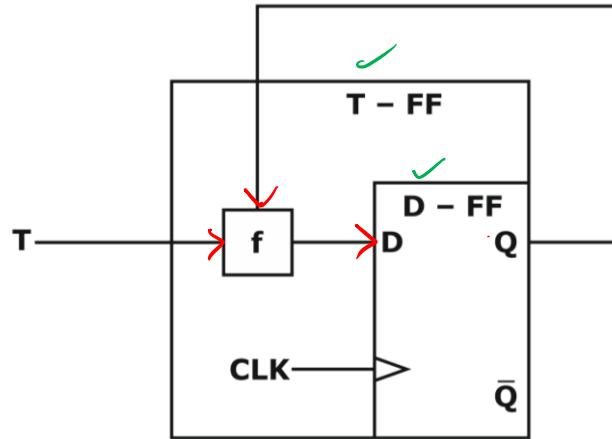

$$Q(t) \\ \textcircled{D} \\ T$$

$$D = Q(t+1)$$

The function f should be

- A. $T \oplus Q$
- B. $T \odot Q$
- C. $T + \bar{Q}$
- D. $T\bar{Q}$


$$Q' T + Q T'$$

$$Q \oplus T$$

Flip flops

| $Q(t)$ | J | K | $Q(t+1)$ | T |
|--------|---|---|----------|-----|
| 0 ✓ | 0 | 0 | 0 ✓ | 0 ✓ |
| 0 ✓ | 0 | 1 | 0 ✓ | 0 ✓ |
| 0 ✓ | 1 | 0 | 1 ✓ | 1 ✓ |
| 0 ✓ | 1 | 1 | 1 ✓ | 1 ✓ |
| 1 ✓ | 0 | 0 | 1 ✓ | 0 ✓ |
| 1 ✓ | 0 | 1 | 0 ✓ | 1 ✓ |
| 1 ✓ | 1 | 0 | 1 ✓ | 0 ✓ |
| 1 ✓ | 1 | 1 | 0 ✓ | 1 ✓ |

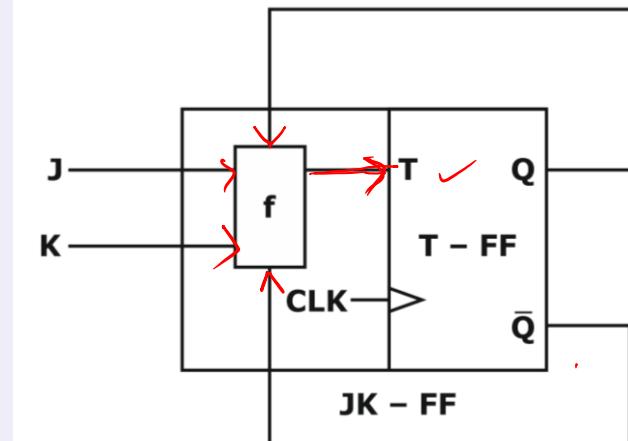2. What should be the function f to make the circuit a JK-FF ?



JK Q

- A. $JQ + K\bar{Q}$
- B. $\bar{J}Q + K\bar{Q}$
- C. $J\bar{Q} + KQ$
- D. None

$$T = \bar{J}K + JQ$$


$$\bar{Q}J\bar{K} + \bar{Q}JK + Q\bar{J}K + QJK$$

$$\bar{Q}J[\bar{K} + K] + QK[J + J]$$

$$\bar{Q}J + QK$$

Flip flops

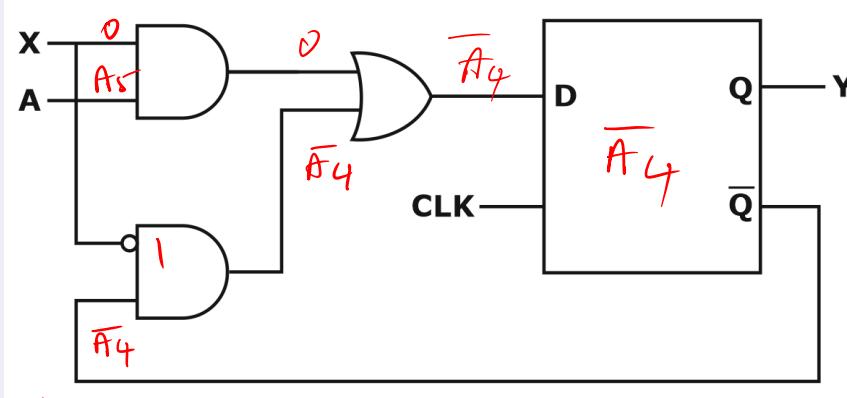3. Consider the following realization with X and A as external control signals. If they are given for 6 clock cycles, what will be the output y ?



- A. \bar{A}_4
- B. A_5
- C. A_3
- D. \bar{A}_3

| CLK | 1 | 2 | 3 | 4 | 5 | 6 |
|-----|-------|-------|-------|-------|-------|-------|
| X | 1 | 0 | 0 | 1 | 1 | 0 |
| A | A_0 | A_1 | A_2 | A_3 | A_4 | A_5 |

Basics of Flip flops

| $Q(t)$ | $Q(t+1)$ | M | N |
|--------|----------|---|---|
| 0 → 0 | 1 X | | |
| 0 → 1 | 0 X | | |
| 1 → 0 | X 0 | | |
| 1 → 1 | X 1 | | |

M N
0 0
1 0 A.
X 0

4. Consider the characteristic table below for MN Flip flop

| M | N | Q(Next) |
|---|---|----------------|
| 0 | 0 | Q (Complement) |
| 0 | 1 | 1 (Set to 1) |
| 1 | 0 | 0 (Clear to 0) |
| 1 | 1 | Q (No change) |

M N
1 1
1 0
1 X

Which of the following denotes the excitation table of the MN flip-flop ?

| <u>Q (PS)</u> | <u>Q (NS)</u> | M | N |
|---------------|---------------|---|---|
| 0 | 0 | 0 | X |
| 0 | 1 | 1 | X |
| 1 | 0 | X | 1 |
| 1 | 1 | X | 0 |

C.

| <u>Q (PS)</u> | <u>Q (NS)</u> | M | N |
|---------------|---------------|---|---|
| 0 | 0 | X | 1 |
| 0 | 1 | 0 | X |
| 1 | 0 | 1 | X |
| 1 | 1 | X | 0 |

| <u>Q (PS)</u> | <u>Q (NS)</u> | M | N |
|---------------|---------------|---|---|
| 0 | 0 | X | 0 |
| 0 | 1 | X | 1 |
| 1 | 0 | 1 | X |
| 1 | 1 | 0 | X |

D.

| <u>Q (PS)</u> | <u>Q (NS)</u> | M | N |
|---------------|---------------|---|---|
| 0 | 0 | 1 | X |
| 0 | 1 | 0 | X |
| 1 | 0 | X | 0 |
| 1 | 1 | X | 1 |